

## CS 61C: Great Ideas in Computer Architecture *Synchronous Digital Systems*


Instructors:

Krste Asanovic & Vladimir Stojanovic

<http://inst.eecs.berkeley.edu/~cs61c/sp15>


1

## You are Here!

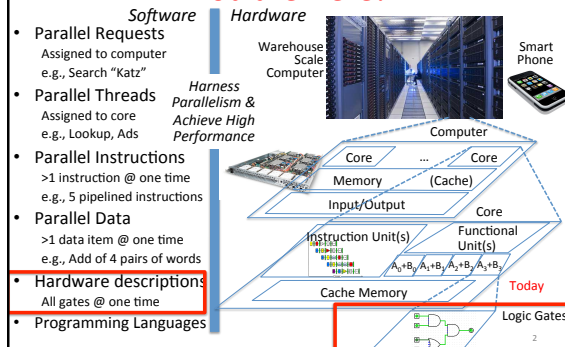

2
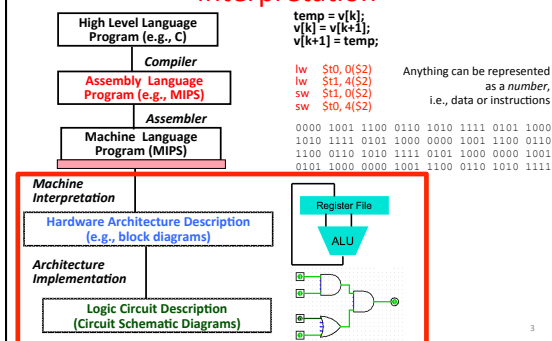
## Levels of Representation/ Interpretation



3

## Hardware Design

- Next several weeks: how a modern processor is built, starting with basic elements as building blocks
- Why study hardware design?
  - Understand capabilities and limitations of HW in general and processors in particular
  - What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
  - Background for more in-depth HW courses (CS 150, CS 152)
  - Hard to know what you'll need for next 30 years
  - There is only so much you can do with standard processors: you may need to design own custom HW for extra performance
    - Even some commercial processors today have customizable hardware!

4

## Synchronous Digital Systems

Hardware of a processor, such as the MIPS, is an example of a Synchronous Digital System

**Synchronous:**

- All operations coordinated by a central clock
  - "Heartbeat" of the system!


**Digital:**

- Represent all values by discrete values
- Two binary digits: 1 and 0
- Electrical signals are treated as 1's and 0's
  - 1 and 0 are complements of each other
- High /low voltage for true / false, 1 / 0

5
 
## Switches: Basic Element of Physical Implementations



- Implementing a simple circuit (arrow shows action if wire changes to "1" or is *asserted*):



6
  
## Switches (cont'd)


- Compose switches into more complex ones (Boolean functions):



7
 
## Historical Note

- Early computer designers built ad hoc circuits from switches
- Began to notice common patterns in their work: ANDs, ORs, ...
- Master's thesis (by Claude Shannon) made link between work and 19<sup>th</sup> Century Mathematician George Boole
  - Called it "Boolean" in his honor
- Could apply math to give theory to hardware design, minimization, ...



8

## Transistors

- High voltage ( $V_{dd}$ ) represents 1, or true
  - In modern microprocessors,  $V_{dd} \sim 1.0$  Volt
- Low voltage (0 Volt or Ground) represents 0, or false
- Pick a midpoint voltage to decide if a 0 or a 1
  - Voltage greater than midpoint = 1
  - Voltage less than midpoint = 0
  - This removes noise as signals propagate – a big advantage of digital systems over analog systems
- If one switch can control another switch, we can build a computer!
- Our switches: CMOS transistors

9


## CMOS Transistor Networks

- Modern digital systems designed in CMOS
  - MOS: Metal-Oxide on Semiconductor
  - C for complementary: use *pairs* of normally-open and normally-closed switches
    - Used to be called COS-MOS for complementary-symmetry - MOS
- CMOS transistors act as voltage-controlled switches
  - Similar, though easier to work with, than electro-mechanical relay switches from earlier era
  - Use energy primarily when switching

10

 
## CMOS Transistors


- Three terminals: source, gate, and drain
  - Switch action: if voltage on gate terminal is (some amount) higher/lower than source terminal then conducting path established between drain and source terminals (switch is closed)



11

## #2: Moore's Law

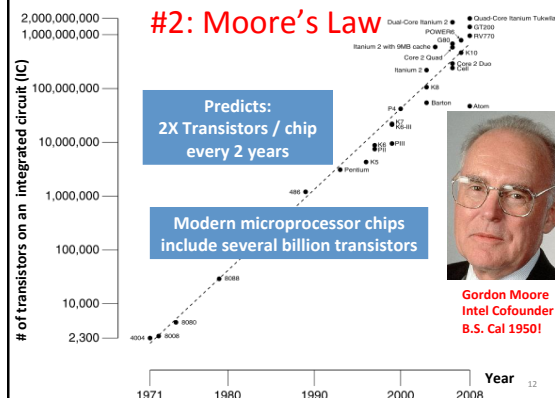

 


### CMOS Circuit Rules

- Don't pass weak values => Use Complementary Pairs
  - N-type transistors pass weak 1's ( $V_{dd} - V_{th}$ )
  - N-type transistors pass strong 0's (ground)
  - Use N-type transistors only to pass 0's (N for negative)
  - Converse for P-type transistors: Pass weak 0s, strong 1s
    - Pass weak 0's ( $V_{th}$ ), strong 1's ( $V_{dd}$ )
    - Use P-type transistors only to pass 1's (P for positive)
  - Use pairs of N-type and P-type to get strong values
- Never leave a wire undriven
  - Make sure there's always a path to  $V_{dd}$  or GND
- Never create a path from  $V_{dd}$  to GND (ground)
  - This would short-circuit the power supply!
 
### CMOS Networks

*p-channel transistor*  
 closed when voltage at Gate is low  
 opens when:  
 voltage(Gate) > voltage (Threshold)




*n-channel transistor*  
 open when voltage at Gate is low  
 closes when:  
 voltage(Gate) > voltage (Threshold)

what is the  
relationship  
between x and y?

x	y
0 Volt (GND)	1 Volt ( $V_{dd}$ )
1 Volt ( $V_{dd}$ )	0 Volt (GND)

Called an *inverter* or *not gate*

### Two-Input Networks

 


what is the  
relationship between x, y and z?

x	y	z
0 Volt	0 Volt	1 Volt
0 Volt	1 Volt	1 Volt
1 Volt	0 Volt	1 Volt
1 Volt	1 Volt	0 Volt

Called a *NAND gate*  
*(NOT AND)*

### Clickers/Peer Instruction

 

x	y	z
0 Volt	0 Volt	0 Volts
0 Volt	1 Volt	0 Volts
1 Volt	0 Volt	0 Volts
1 Volt	1 Volt	1 Volts

### Administrivia

- Project 1-1 is out - due 3/01
  - See Sagar @ end of lec. if you still don't have team
- Midterm is next Thursday 2/26, in class
  - Covers up to and including the previous lecture
  - 1 handwritten, double sided, 8.5"x11" cheat sheet
  - We'll give you MIPS green sheet
  - DSP: Should have received email from Sagar this morning
  - Conflicts/DSP must email/respond by tomorrow (Weds.) @ 23:59:59

## Administrivia


- Review Sessions:
  - TA: Probably 2/23, 6-8pm, waiting for room reservation
  - HKN: Saturday 2/21, 1-4pm, 100 GPB

19

## Combinational Logic Symbols

- Common combinational logic systems have standard symbols called logic gates


- Buffer, NOT

 

- AND, NAND




- OR, NOR

 

Inverting versions (NOT, NAND, NOR) easiest to implement with CMOS transistors (the switches we have available and use most)

20

## Truth Tables for Combinational Logic

 

Exhaustive list of the output value generated for each combination of inputs

a	b	c	d	y
0	0	0	0	F(0,0,0,0)
0	0	0	1	F(0,0,0,1)
0	0	1	0	F(0,0,1,0)
0	0	1	1	F(0,0,1,1)
0	1	0	0	F(0,1,0,0)
0	1	0	1	F(0,1,0,1)
0	1	1	0	F(0,1,1,0)
0	1	1	1	F(0,1,1,1)
1	0	0	0	F(1,0,0,0)
1	0	0	1	F(1,0,0,1)
1	0	1	0	F(1,0,1,0)
1	0	1	1	F(1,0,1,1)
1	1	0	0	F(1,1,0,0)
1	1	0	1	F(1,1,0,1)
1	1	1	0	F(1,1,1,0)
1	1	1	1	F(1,1,1,1)

21


## Truth Table Example #1:

$y = F(a,b)$ : 1 iff  $a \neq b$

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

22

## Truth Table Example #2: 2-bit Adder

 

How Many Rows?

A	B	C
$a_1 a_0$	$b_1 b_0$	$c_2 c_1 c_0$

23

## Truth Table Example #3: 32-bit Unsigned Adder

A	B	C
000 ... 0	000 ... 0	000 ... 00
000 ... 0	000 ... 1	000 ... 01
.	.	.
.	.	.
.	.	.
111 ... 1	111 ... 1	111 ... 10

How Many Rows?

24

### Truth Table Example #4: 3-input Majority Circuit

$Y =$

This is called *Sum of Products* form;  
Just another way to represent the TT  
as a logical expression

More simplified forms  
(fewer gates and wires)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


25

### Boolean Algebra

- Use plus "+" for OR  
– "logical sum"
- Use product for AND ( $a \cdot b$  or implied via  $ab$ )  
– "logical product"
- "Hat" to mean complement (NOT)
- Thus  
 $ab + a + \bar{c}$   
 $= a \cdot b + a + \bar{c}$   
 $= (a \text{ AND } b) \text{ OR } a \text{ OR } (\text{NOT } c)$

26
 
### Boolean Algebra: Circuit & Algebraic Simplification



original circuit

equation derived from original circuit

algebraic simplification

simplified circuit

27

### Laws of Boolean Algebra

$X\bar{X} = 0$	$X + \bar{X} = 1$	Complementarity
$X0 = 0$	$X + 1 = 1$	Laws of 0's and 1's
$X1 = X$	$X + 0 = X$	Identities
$XX = X$	$X + X = X$	Idempotent Laws
$XY = YX$	$X + Y = Y + X$	Commutativity
$(X Y) Z = Z (Y Z)$	$(X + Y) + Z = Z + (Y + Z)$	Associativity
$X(Y + Z) = XY + XZ$	$X + YZ = (X + Y)(X + Z)$	Distribution
$X Y + X = X$	$(X + Y) X = X$	Uniting Theorem
$\bar{X} Y + X = X + Y$	$(\bar{X} + Y) X = X Y$	United Theorem v. 2
$\bar{X} \bar{Y} = \overline{X + Y}$	$\overline{X + Y} = \bar{X} \bar{Y}$	DeMorgan's Law

28

### Boolean Algebraic Simplification Example

$$y = ab + a + c$$

29

### Boolean Algebraic Simplification Example

$$\begin{aligned}
 y &= ab + a + c \\
 abc y &= a(b + 1) + c && \text{distribution, identity} \\
 0000 &= a(1) + c && \text{law of 1's} \\
 0011 &= a + c && \text{identity} \\
 0100 & && \\
 0111 & && \\
 1001 & && \\
 1011 & && \\
 1101 & && \\
 1111 & &&
 \end{aligned}$$

30

### Clickers/Peer Instruction

- Simplify  $Z = A + BC + \overline{A} \cdot \overline{(BC)}$
- A:  $Z = 0$
- B:  $Z = A(1 + BC)$
- C:  $Z = \overline{(A + BC)}$
- D:  $Z = BC$
- E:  $Z = 1$


31

### In the News: Spy Games


- Russian security firm claims US spy agencies insert code into disk drive firmware to snoop on foreign computers
- Also, attacks computers not connected to internet by secreting hardware that can listen to long-wave radio broadcasts
- Or through infected USB drives

32


### Signals and Waveforms

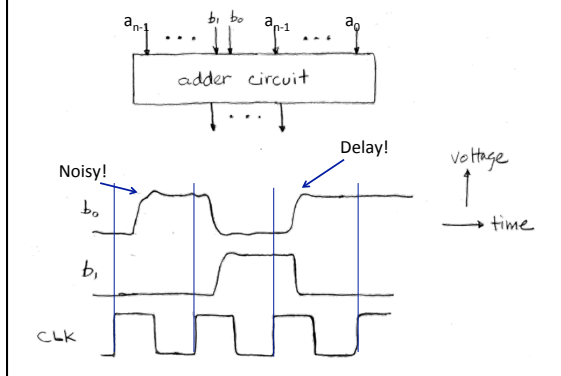


### Signals and Waveforms: Grouping

 

### Signals and Waveforms: Circuit Delay

 

### Sample Debugging Waveform

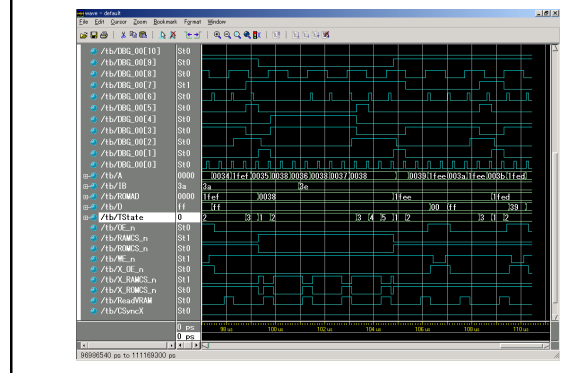

## Type of Circuits

- *Synchronous Digital Systems* consist of two basic types of circuits:
  - Combinational Logic (CL) circuits
    - Output is a function of the inputs only, not the history of its execution
    - E.g., circuits to add A, B (ALUs)
  - Sequential Logic (SL)
    - Circuits that “remember” or store information
    - aka “State Elements”
    - E.g., memories and registers (Registers)

37


## Uses for State Elements

- Place to store values for later re-use:
  - Register files (like \$1-\$31 in MIPS)
  - Memory (caches and main memory)
- *Help control flow of information between combinational logic blocks*
  - State elements hold up the movement of information at input to combinational logic blocks to allow for orderly passage

38
 
## Accumulator Example

Why do we need to control the flow of information?




Want:  $S=0$ ;  
 for ( $i=0; i<n; i++$ )  
      $S = S + X_i$

Assume:

- Each X value is applied in succession, one per cycle
- After n cycles the sum is present on S

39

## First Try: Does this work?

 


No!

Reason #1: How to control the next iteration of the ‘for’ loop?


Reason #2: How do we say: ‘S=0’?

40

## Second Try: How About This?

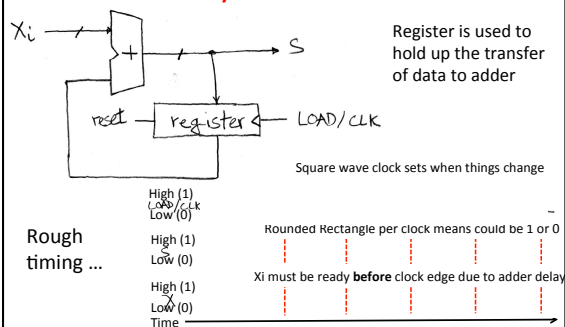


## Model for Synchronous Systems

 

- Collection of Combinational Logic blocks separated by registers
- Feedback is optional
- Clock signal(s) connects only to clock input of registers
- Clock (CLK): steady square wave that synchronizes the system
- Register: several bits of state that samples on rising edge of CLK (positive edge-triggered) or falling edge (negative edge-triggered)

42

### Register Internals

 

- $n$  instances of a “Flip-Flop”
- **Flip-flop** name because the output flips and flops between 0 and 1
- $D$  is “data input”,  $Q$  is “data output”
- Also called “D-type Flip-Flop”

43

### Camera Analogy Timing Terms

- Want to take a portrait – timing right before and after taking picture
- **Set up time** – don’t move since about to take picture (open camera shutter)
- **Hold time** – need to hold still after shutter opens until camera shutter closes
- **Time click to data** – time from open shutter until can see image on output (viewscreen)

44


### Hardware Timing Terms

- **Setup Time**: when the input must be stable *before* the edge of the CLK
- **Hold Time**: when the input must be stable *after* the edge of the CLK
- **“CLK-to-Q” Delay**: how long it takes the output to change, measured from the edge of the CLK

45
 
### Maximum Clock Frequency

- What is the maximum frequency of this circuit?



Hint:  
Frequency =  $1/\text{Period}$

Max Delay = Setup Time + CLK-to-Q Delay + CL Delay

46

### And in Conclusion, ...

- Multiple Hardware Representations
  - Analog voltages quantized to represent logic 0 and logic 1
  - Transistor switches form gates: AND, OR, NOT, NAND, NOR
  - Truth table mapped to gates for combinational logic design
  - Boolean algebra for gate minimization
- State Machines
  - Finite State Machines: made from **Stateless** combinational logic and **Stateful** “Memory” Logic (aka Registers)
  - Clocks synchronize D-FF change (Setup and Hold times important!)

47